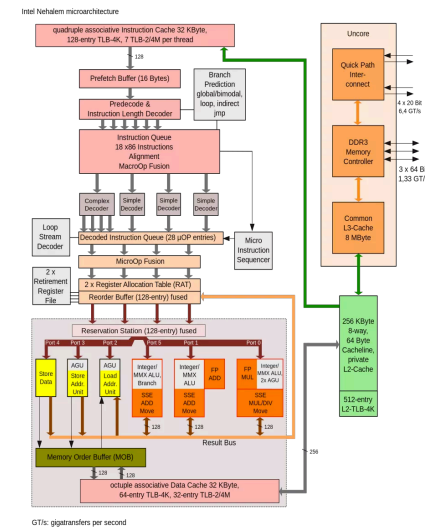


# CSC 411

## Computer Organization (Spring 2022) Lecture 15: Basics of logic design (Appendix)

Prof. Marco Alvarez, University of Rhode Island

## Goal of Chapter 4



## Transistors


- Building block of computers
- ICs contain billions
- Transistors act as switches
  - can be combined to implement simple logic gates
  - AND OR NOT
- Two types of MOS transistors
  - metal-oxide semiconductors



## Moore's Law: The number of transistors on microchips doubles every two years

Moore's law describes the empirical regularity that the number of transistors on integrated circuits doubles approximately every two years. This advancement is important for other aspects of technological progress in computing – such as processing speed or the price of computers.

### Transistor count

 

Data source: Wikipedia (wikipedia.org/wiki/Transistor\_count)  
OurWorldInData.org – Research and data to make progress against the world's largest problems. Licensed under CC-BY by the authors Hannah Ritchie and Max Roser.

## NOT Gate



This is actually the CMOS NOT Gate

Why do we call it NOT?

- If  $A = 0V$  then  $Y = 3V$
- If  $A = 3V$  then  $Y = 0V$

**Digital circuit:** one possible interpretation

  - Interpret **0V** as logical (binary) **0** value
- Interpret **3V** as logical (binary) **1** value





**Truth table:** shows what is the logical output of the circuit for each possible input

A	Y
0	1
1	0

[https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign\\_comparch-2021-lecture4-combinational-logic-afterlecture.pdf](https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign_comparch-2021-lecture4-combinational-logic-afterlecture.pdf)


## NAND Gate

Let's build more complex gates!

  


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 
[https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign\\_comparch-2021-lecture4-combinational-logic-afterlecture.pdf](https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign_comparch-2021-lecture4-combinational-logic-afterlecture.pdf)






A	Y
0	1
1	0

 

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

   

[https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign\\_comparch-2021-lecture4-combinational-logic-afterlecture.pdf](https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign_comparch-2021-lecture4-combinational-logic-afterlecture.pdf)


## Common logic gates

**Buffer**

 

A	Z
0	0
1	1

**AND**

 

A	B	Z
0	0	0
0	1	0
1	0	0
1	1	1

**OR**



A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

**XOR**




A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

**Inverter**



A	Z
0	1
1	0

**NAND**

 

A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0

**NOR**



A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0

**XNOR**



A	B	Z
0	0	1
0	1	0
1	0	0
1	1	1

[https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign\\_comparch-2021-lecture4-combinational-logic-afterlecture.pdf](https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign_comparch-2021-lecture4-combinational-logic-afterlecture.pdf)

## Building logic circuits


Now, we understand the workings of the basic logic gates

What is our next step?

Build some of the logic structures that are important components of the microarchitecture of a computer!

A logic circuit is composed of:

- Inputs
- Outputs

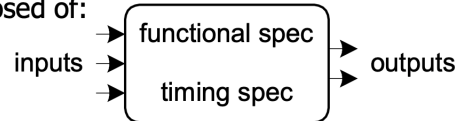


*Functional specification* (describes relationship between inputs and outputs)

*Timing specification* (describes the delay between inputs changing and outputs responding)

[https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign\\_comparch-2021-lecture4-combinational-logic-afterlecture.pdf](https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign_comparch-2021-lecture4-combinational-logic-afterlecture.pdf)

## Types of logic circuits

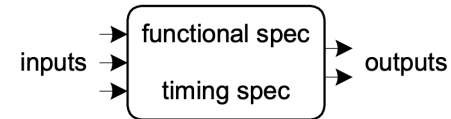

### Combinational Logic

- Memoryless
- Outputs are strictly dependent on the combination of input values that are being applied to circuit *right now*
- In some books called Combinatorial Logic

### Later we will learn: Sequential Logic

- Has memory
  - Structure stores history → Can "store" data values
- Outputs are determined by previous (historical) and current values of inputs


[https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign\\_comparch-2021-lecture4-combinational-logic-afterlecture.pdf](https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign_comparch-2021-lecture4-combinational-logic-afterlecture.pdf)

## Disclaimer


Some of the following slides are adapted from:

Computer Organization and Design (Patterson and Hennessy)

The Hardware/Software Interface

 

## 3-bit decoder

 


a. A 3-bit decoder

Inputs			Outputs							
12	11	10	Out7	Out6	Out5	Out4	Out3	Out2	Out1	Out0
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

b. The truth table for a 3-bit decoder
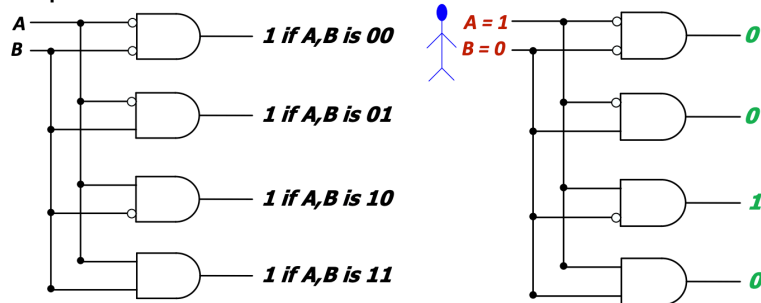
## Decoder


- $n$  inputs and  $2^n$  outputs
- Exactly one of the outputs is 1 and all the rest are 0s
- The **one output** that is logically 1 is the output corresponding to the input **pattern** that the logic circuit is expected to detect



[https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign\\_comparch-2021-lecture4-combinational-logic-afterlecture.pdf](https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign_comparch-2021-lecture4-combinational-logic-afterlecture.pdf)
 
## Decoder

- The decoder is useful in determining how to interpret a bit pattern
  - It could be the **address of a row in DRAM**, that the processor intends to read from
  - It could be an **instruction in the program** and the processor has to decide what action to do! (based on **instruction opcode**)




[https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign\\_comparch-2021-lecture4-combinational-logic-afterlecture.pdf](https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign_comparch-2021-lecture4-combinational-logic-afterlecture.pdf)

## Multiplexor

- **Selects** one of the  $N$  inputs to connect it to the output
  - based on the value of a  $\log_2 N$ -bit control input called **select**
- Example: 2-to-1 MUX


S	D <sub>1</sub>	D <sub>0</sub>	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 


[https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign\\_comparch-2021-lecture4-combinational-logic-afterlecture.pdf](https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign_comparch-2021-lecture4-combinational-logic-afterlecture.pdf)
 
## Multiplexor

- **Selects** one of the  $N$  inputs to connect it to the output
  - based on the value of a  $\log_2 N$ -bit control input called **select**
- Example: 2-to-1 MUX



 
[https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign\\_comparch-2021-lecture4-combinational-logic-afterlecture.pdf](https://safari.ethz.ch/digitaltechnik/spring2021/lib/exe/fetch.php?media=onur-digitaldesign_comparch-2021-lecture4-combinational-logic-afterlecture.pdf)




a. A 32-bit wide 2-to-1 multiplexor

b. The 32-bit wide multiplexor is actually an array of 32 1-bit multiplexors

## 1-bit logical unit for AND and OR

 

## 1-bit adder

 


$$Sum = (a \cdot \bar{b} \cdot \overline{CarryIn}) + (\bar{a} \cdot b \cdot \overline{CarryIn}) + (\bar{a} \cdot \bar{b} \cdot CarryIn) + (a \cdot b \cdot CarryIn)$$

$$CarryOut = (b \cdot CarryIn) + (a \cdot CarryIn) + (a \cdot b)$$


Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{two}$
0	0	1	0	1	$0 + 0 + 1 = 01_{two}$
0	1	0	0	1	$0 + 1 + 0 = 01_{two}$
0	1	1	1	0	$0 + 1 + 1 = 10_{two}$
1	0	0	0	1	$1 + 0 + 0 = 01_{two}$
1	0	1	1	0	$1 + 0 + 1 = 10_{two}$
1	1	0	1	0	$1 + 1 + 0 = 10_{two}$
1	1	1	1	1	$1 + 1 + 1 = 11_{two}$

## Adder hardware for CarryOut

 


$$CarryOut = (b \cdot CarryIn) + (a \cdot CarryIn) + (a \cdot b)$$


## 1-bit ALU (AND, OR, Add)

 


## 32-bit ALU

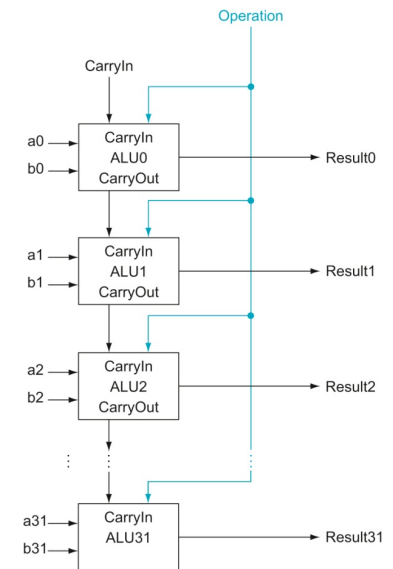

## 1-bit ALU (AND, OR, Add, Sub)

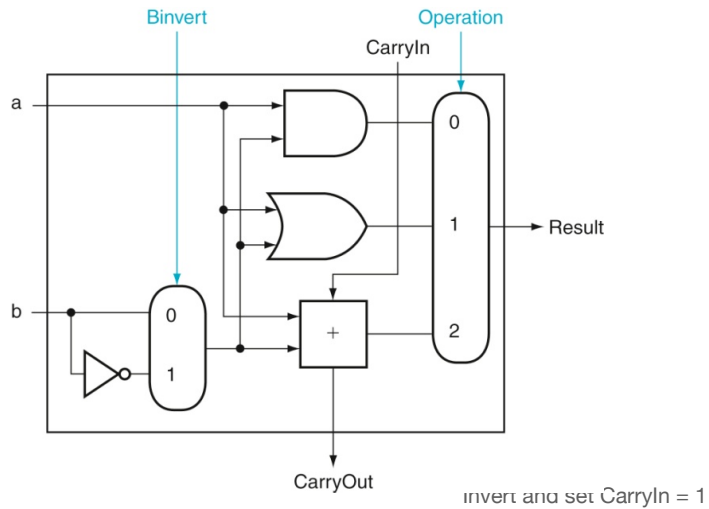


## 1-bit ALU (AND, OR, Add, Sub, NOR)

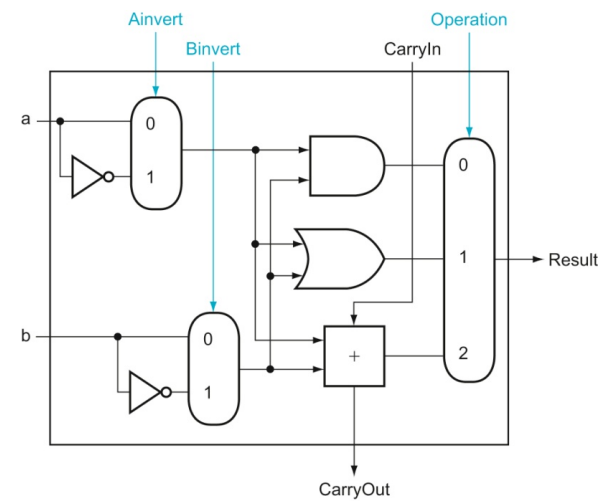

(Top) A 1-bit ALU


(Bottom) a 1-bit ALU for the most significant bit.

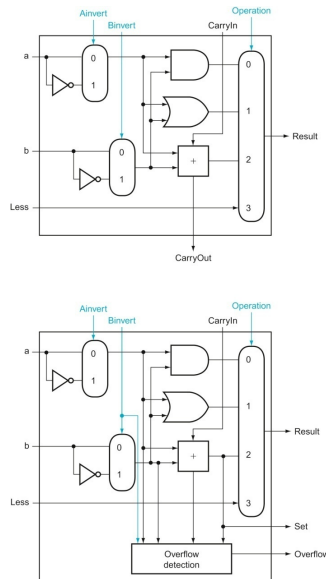The top drawing includes a direct input that is connected to perform the set on less than operation; the bottom has a direct output from the adder for the less than comparison called Set.



## 32-bit ALU

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract

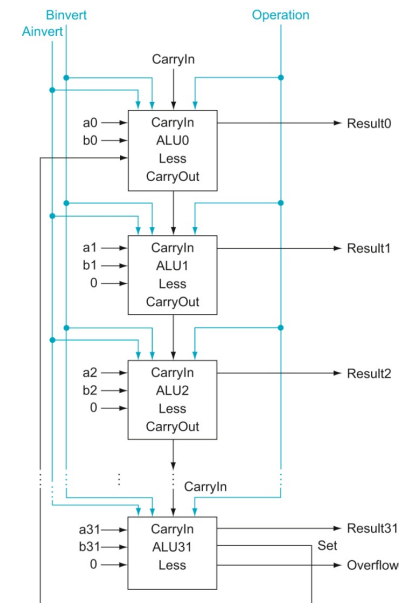

## Adding a zero detector

